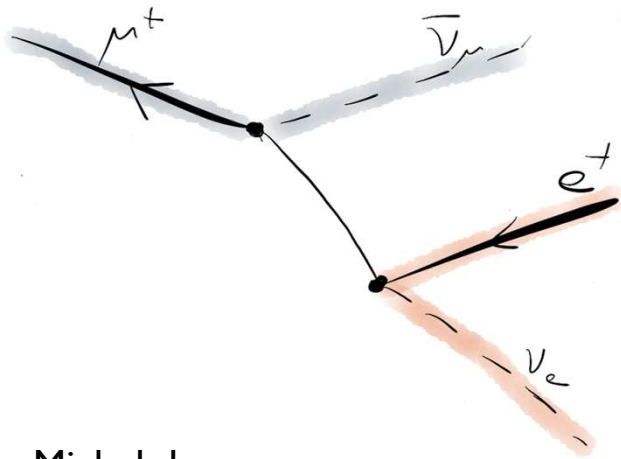




DEVELOPMENT OF A DC-DC CONVERTER FOR THE MU3E EXPERIMENT

MOTIVATION




Michel decay


- Branching ratio nearly $\sim 100\%$
- $\mu \rightarrow eee$ suppressed in the standard model
→ lepton flavour violation



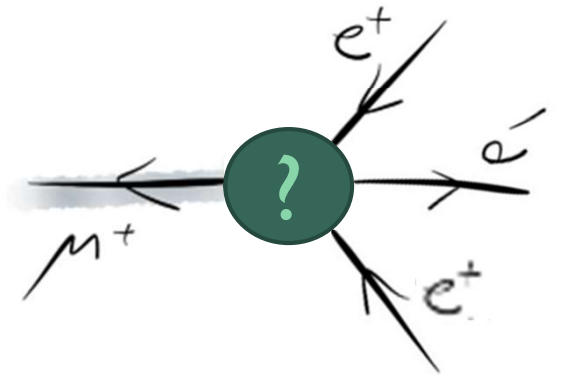Theories of physics
beyond the
standard model



THE EXPERIMENT

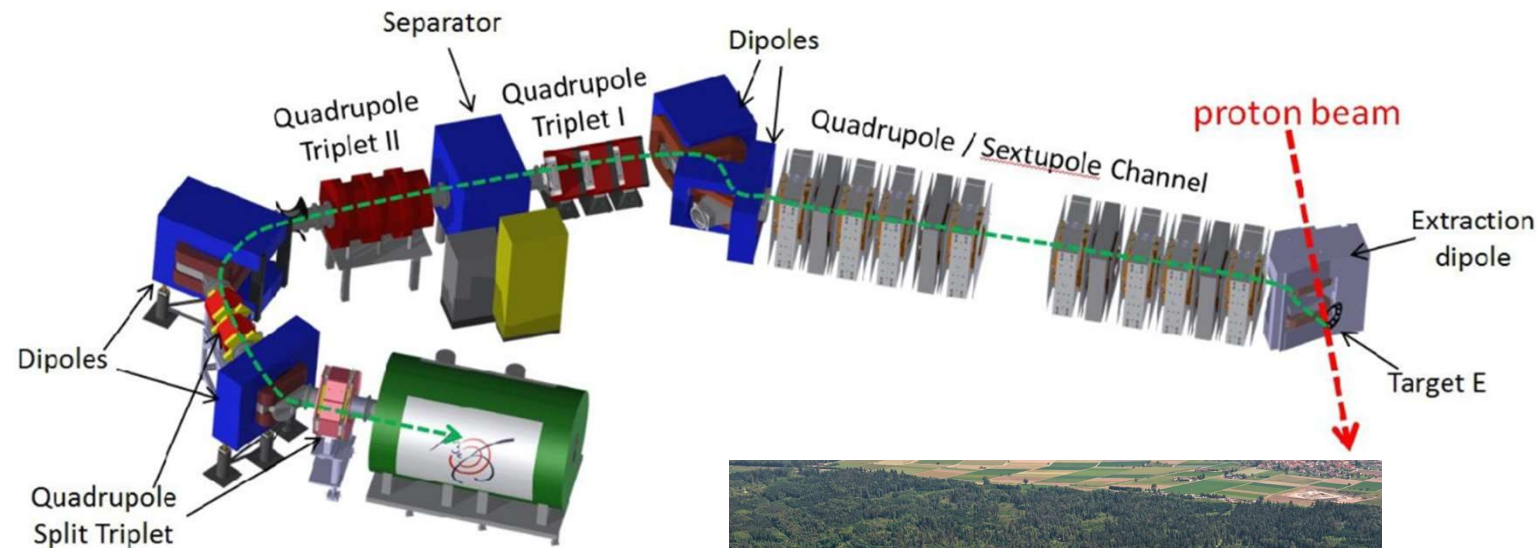


- High intensity muon beam
 - $10^7 - 10^8$ muons/seconds
- Sensitivity goal:
 $B(\mu \rightarrow eee) \leq 2 \cdot 10^{-15}$



Paul Scherrer Institute,
Villigen, Switzerland

THE DETECTOR

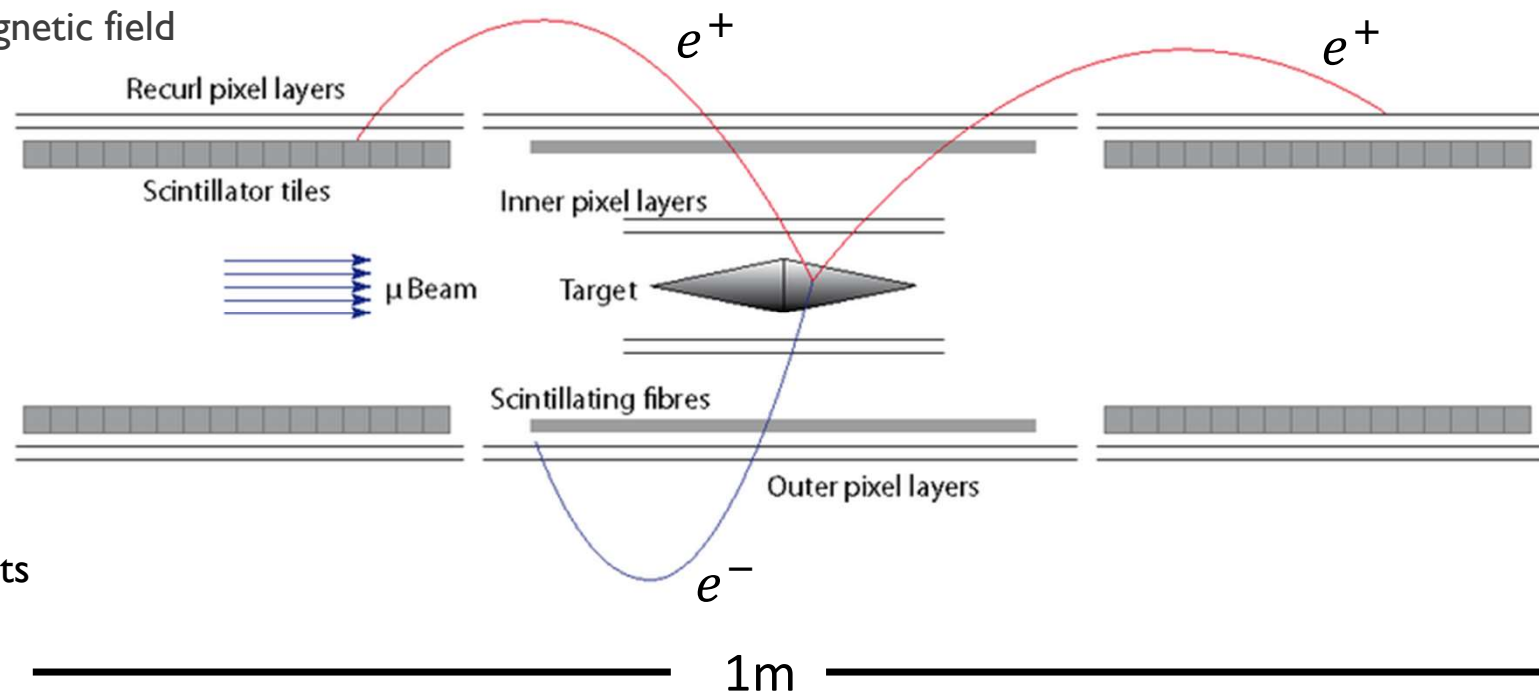- Placed inside a IT strong magnetic field
- Three detector subsystems



- Pixel detector (MuPix sensors)
 - Accurate track and vertex reconstruction

- Scintillating fibres
 - Scintillating tiles
- } Exact timing measurements

POWER REQUIREMENTS



- Relatively low voltages required by the detector components (1-3.3V)
- Cables are very long → high losses through the cables
- Thicker cables are not possible according to size
- Solution: DC-DC converters close to the detector parts step a 20V input power down to the required value
- Power distribution is segmented into power partitions:



- One converter per power partition
- 126 in total
- provide more than **9kW** power in total!


THE MU3E DCDC CONVERTER

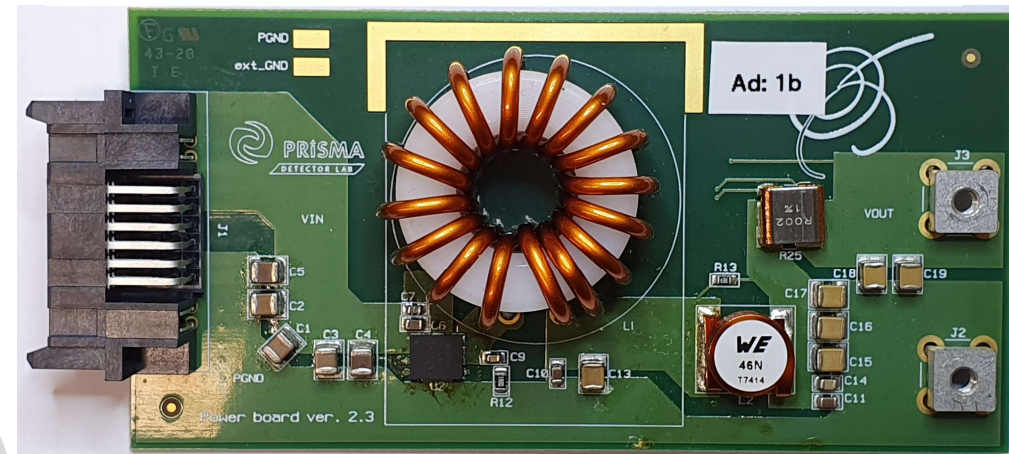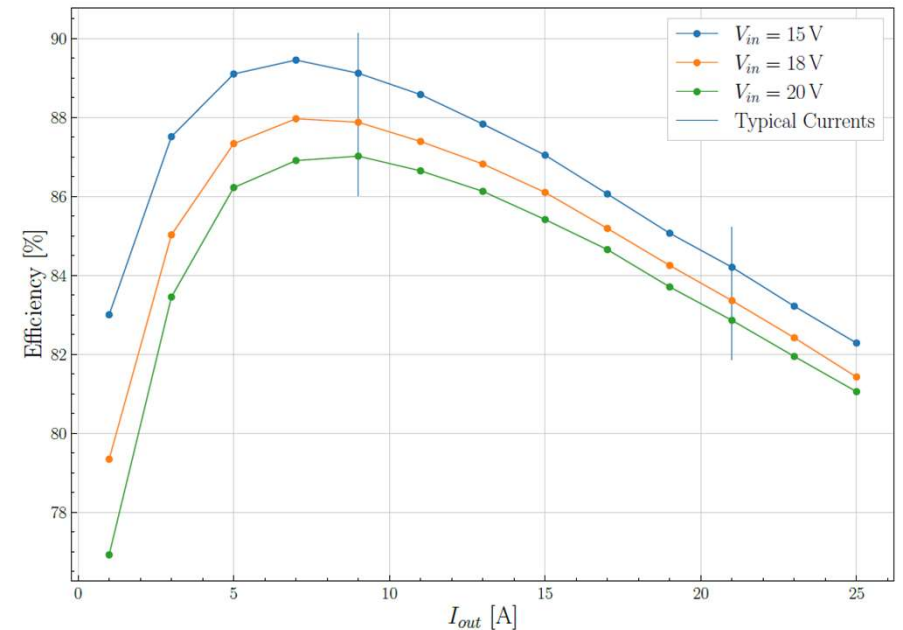- $V_{in} = 20V$
- $V_{out} = 2.1V$
- Working in magnetic field
- $L = 0.55\mu H$
- $C = 22\mu F$
- $f_{switch} = 1MHz$
- Efficiency: 87.0% at 10A





OUTPUT SIGNAL & FILTERING

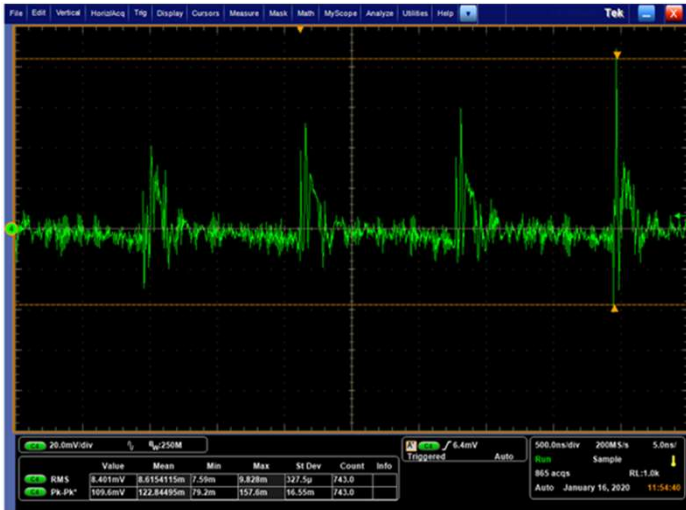$V_{in} = 20V$
 $V_{out} = 2.1V$
 $I_{out} = 5A$
 $f_{sw} = 1MHz$





➔ Output filter required

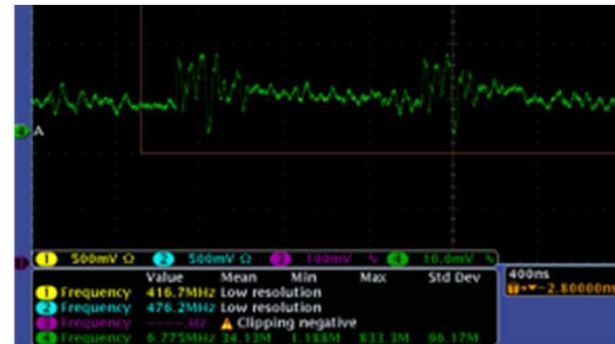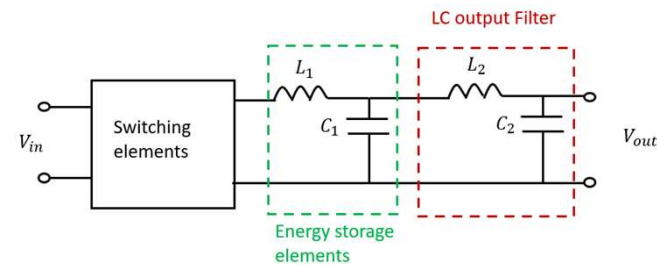


- Total ripple height: ~30mV
- Requirement from MuPlex sensor: $\leq 10mV$

- Ripple high: ~15mV
➔ reduction of 50%
- Not below 10mV
- Rethink filter design

SIMULATION & LAB MEASUREMENTS

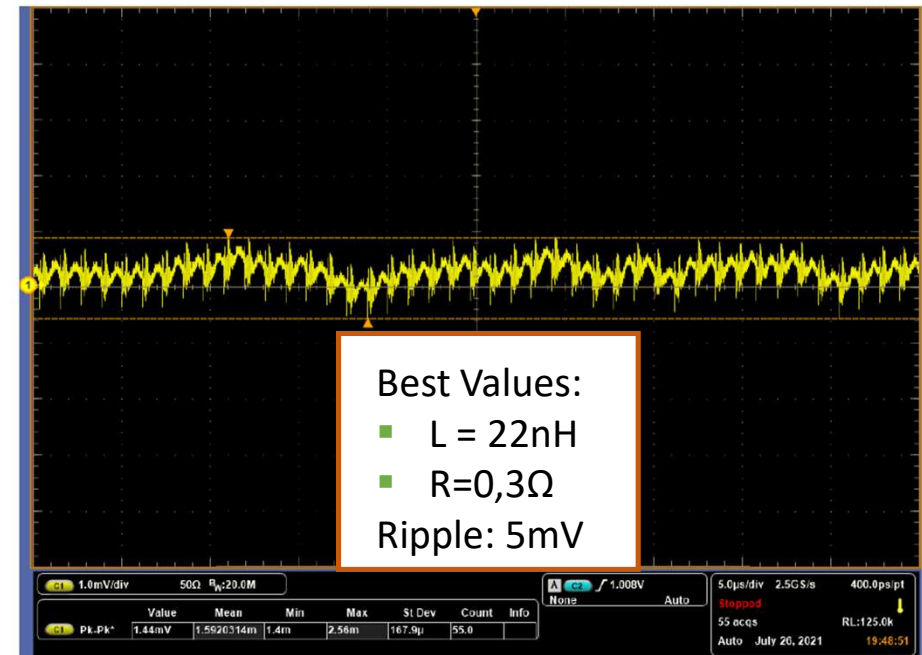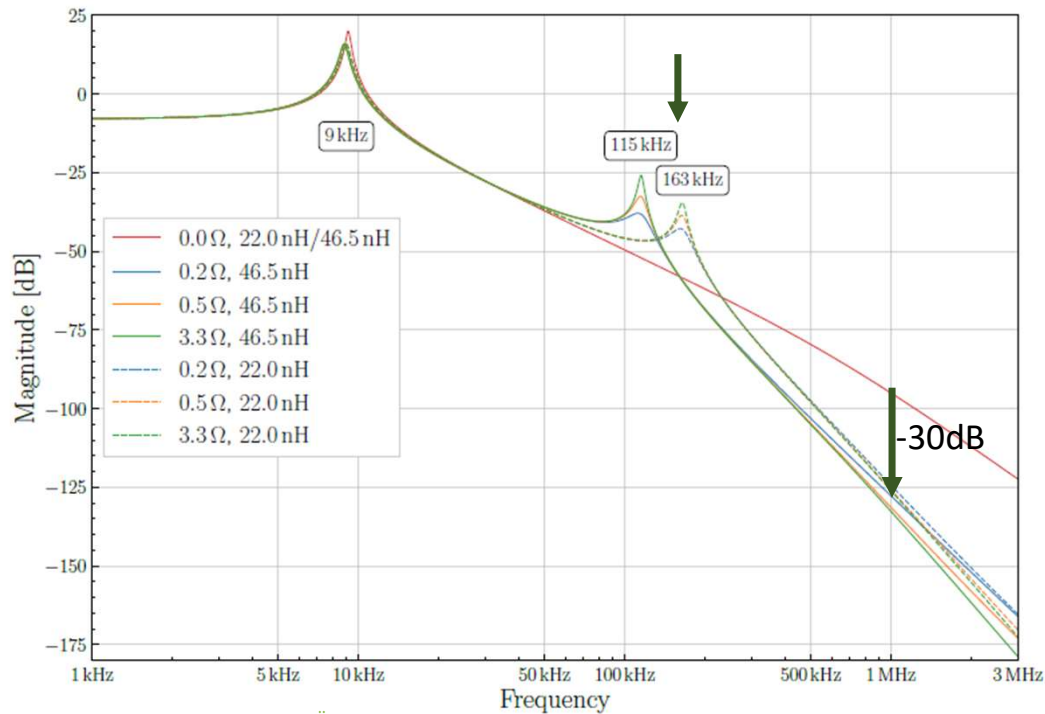


VOLTAGE DROPS

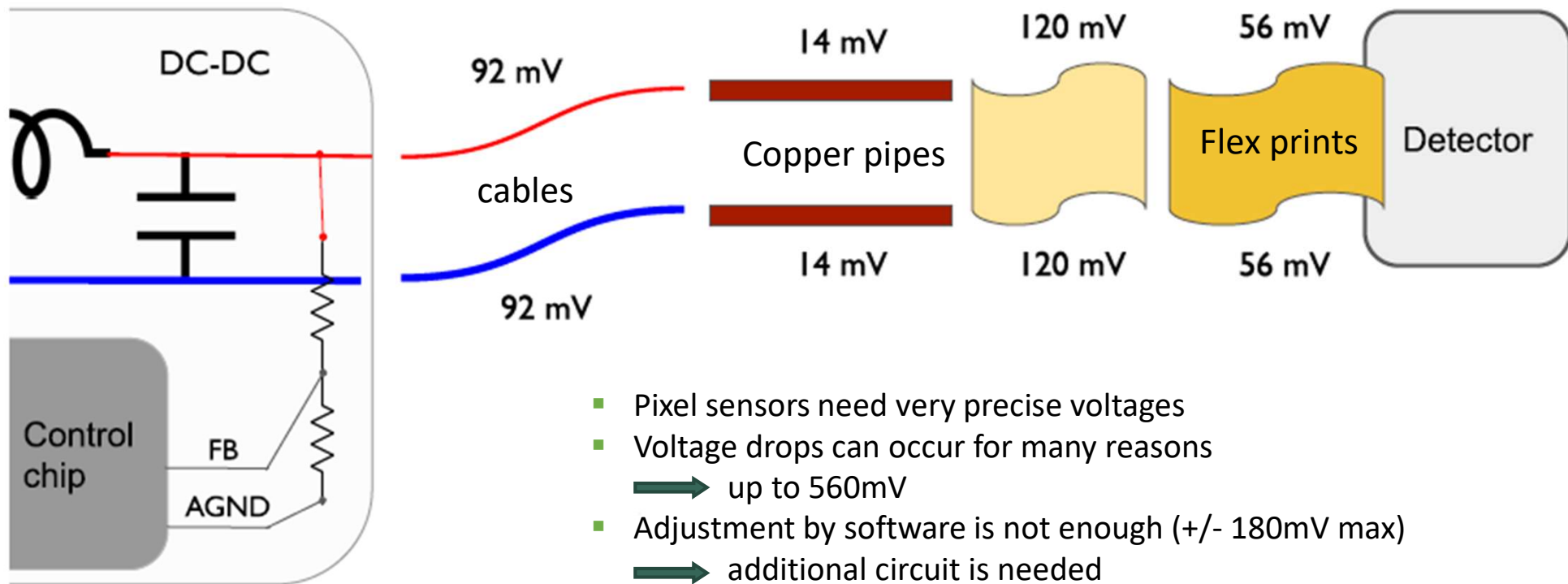

VOLTAGE DROP COMPENSATION


DC/DC Converter Output Stage

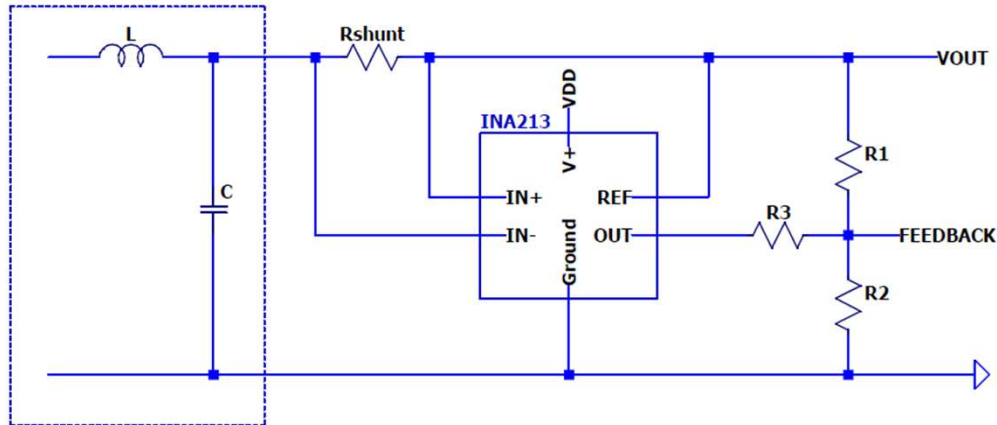

- Output voltage increases linearly with the output current

But:

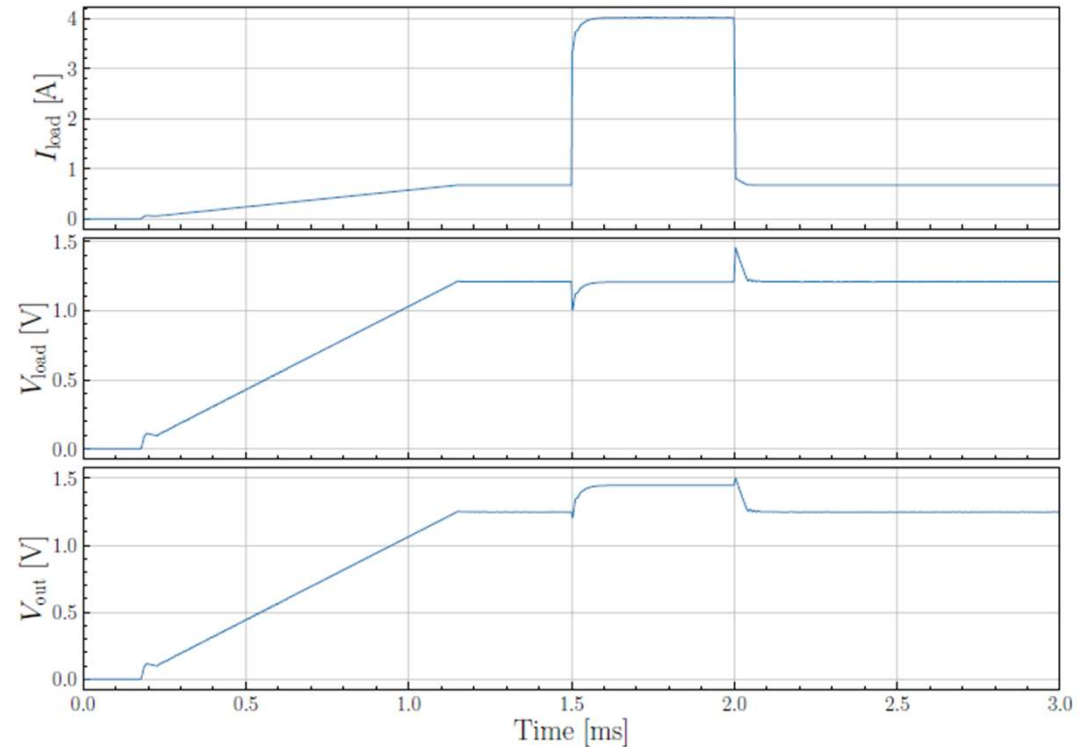- FB circuit is very sensitive to noise
- Resistance of cables must be well known





CONCLUSION

- DCDC converter with
 - Good efficiency
 - Ability to react to voltage drops
 - Very low output ripples
- Next steps
 - Reduce high frequency noise (PCB design)
 - Use converters in a test beam